

**Birla Institute of Technology and Science Pilani (Rajasthan)**  
**EEE F111, ELECTRICAL SCIENCES**  
**First Semester 2025-26**  
**Comprehensive Examination (Close Book-Regular)**

**Date : 13/12/2025 (AN)**


**Duration: 3 Hrs.**

**Max. Marks: 135**


**Note: Attempt all parts of particular question at one place (in sequence). Encircle the final answers.**

**Q1:**

**(A)** Given the circuit shown in Fig. 1, find  $i(t)$  and  $v(t)$  for  $t > 0$  i.e. after the switch is closed. (First calculate the initial conditions, type of response and then proceed). **[15 M]**

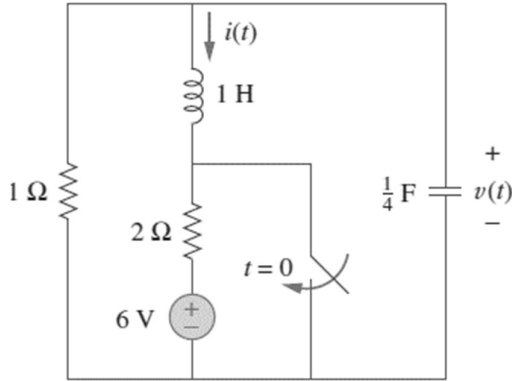

**Fig. 1**

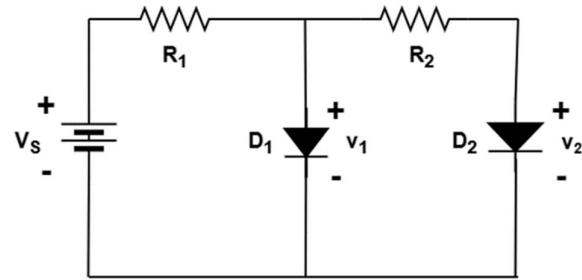

**Fig. 2**

**(B)** Suppose that a filter has gain  $|H(j\omega)| = \frac{16\omega}{(\omega^2 + 4)}$ . (i) For what value of  $\omega$  is the gain maximum?  
(ii) What is the maximum value of the gain? (iii) What are the half-power frequencies? (iv) What is the bandwidth of the filter? **[3 + 2 + 3 + 2 = 10M]**

**Q2:**

**(A)** For the circuit shown in Fig. 2,  $V_s = 8V$  and both the silicon diodes have a saturation current of 1 nA at 300 K.


- (a) Find  $R_2$  for the case that  $R_1 = 20 k\Omega$  and  $v_1 = 0.66 V$ .  
(b) Find  $R_1$  for the case that  $R_2 = 200 \Omega$  and  $v_2 = 0.66 V$ .  
(c) Find  $R_1$  and  $R_2$  for the case that  $v_1 = 0.68 V$  and  $v_2 = 0.66 V$ .

**[15 M]**

**(B)** The silicon BJT in the circuit shown in Fig. 3, has  $\beta = 100$ . Suppose that  $R_1 = 30 k\Omega$ ,  $R_2 = 20 k\Omega$ ,  $R_C = 3 k\Omega$ , and  $i_C = 2.6 mA$ . Determine the following:

- (a) Draw the equivalent circuit diagram showing base resistance  $R_B$  in the common-emitter configuration  
(b)  $R_E$   
(c)  $V_{CE}$  and region of operation

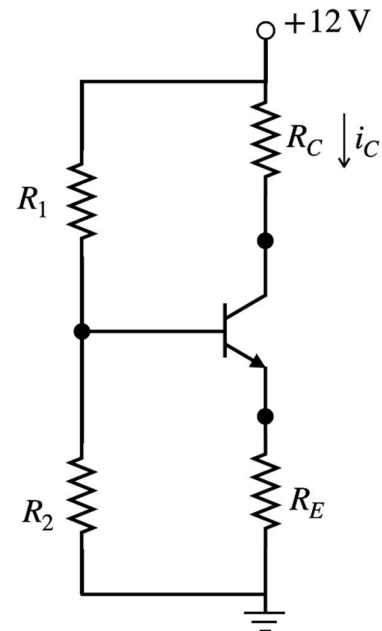**[15 M]**

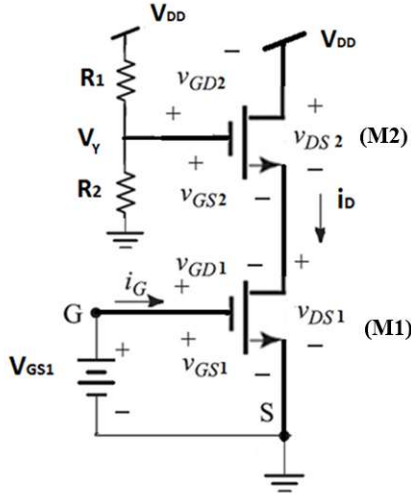
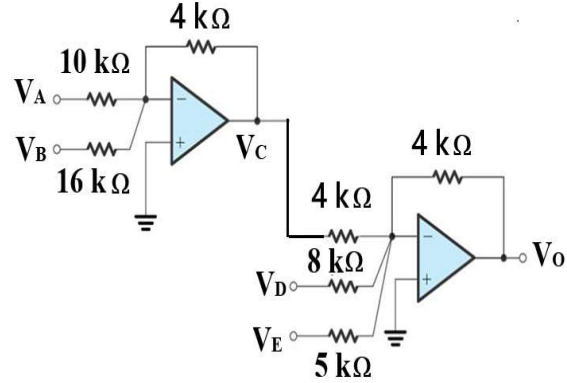


**Fig. 3**

**Q3:**

(A) For the circuit shown in Fig. 4, M1 and M2 MOSFETs have  $I_{DSS} = 1 \text{ mA}$ ,  $V_{GS1} = 2 \text{ V}$ ,  $R_1 = 1000 \text{ K}\Omega$ ,  $R_2 = 800 \text{ K}\Omega$  and  $V_P = -1 \text{ V}$ ,  $V_{DD} = 18 \text{ V}$ . Assuming both the MOSFETs are in active region find (i)  $i_D$  (ii)  $V_{GS2}$ ,  $V_{GD2}$  and  $V_{DS2}$  (iii)  $V_{DS1}$ . Also confirm the region of operation of the MOSFETs M1 and M2 with justification. [15 M]

(B) For the ideal OPAMP circuit shown in Fig. 5 find expression for  $V_C$  and  $V_O$ , in terms of inputs  $V_A$ ,  $V_B$ ,  $V_D$ , and  $V_E$ . (show all steps) [10 M]

**Fig. 4****Fig. 5****Q4:**


(A) A 50 Hz, three-phase Y-connected 400 V (rms-line) balanced source supplies a  $\Delta$ -connected three phase balanced load at power factor of 0.8 lagging. The power drawn by per-phase load (Z) is 2 kVA. Calculate:

- Per-phase load parameters (R and X)
- RMS phase and line current of load
- Three-phase active and reactive power drawn by load
- Load power factor if supply frequency is changed to 60 Hz

**[16 M]**

(B) A magnetic iron core with a relative permeability of 2000 is as shown in Fig. 6. The core has an air-gap of 2 mm. (Given:  $\mu_0 = 4\pi \times 10^{-7} \text{ Wb/A-m}$ , all other parameters are depicted on figure itself). Calculate:

- Reluctances of magnetic core, air-gap (without fringing effect) and overall magnetic circuit
- Number of turns (N) required in coil to produce a flux of 2 mWb
- Draw a properly labelled neat and clean electrical analogous circuit diagram.

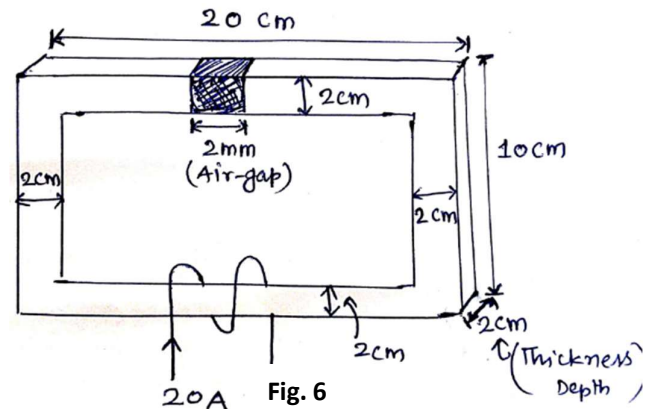**[15 M]****Fig. 6****Q5:**

(a) Calculate the phase difference between  $v_1 = -10 \cos(\omega t + 50^\circ)$  and  $v_2 = 12 \sin(\omega t - 10^\circ)$ . State which sinusoid is leading. [3 M]

(b) For the circuit shown in Fig. 7, find  $v_o$  when ' $i_s$ ' is 30 A.

[3 M]

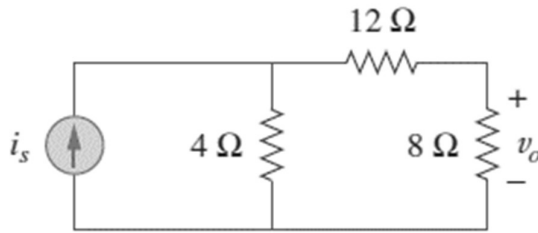


Fig. 7

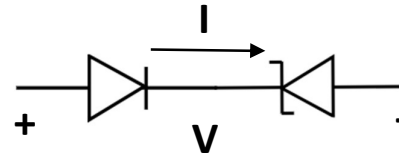


Fig. 8

(c) Consider the diode circuit as shown in Fig. 8. Sketch the I-V characteristics for a voltage sweep of -7 V to +7 V. Assume the reverse breakdown voltage of the Zener diode and conventional PN diode is 6 V and 24 V, respectively. Also consider a 0.7 V voltage drop across both diodes when current flows in the forward direction and zero ON resistance. [3 M]

(d) For solving the following question make the following table in your **answer-sheet** and write only the final answers with proper units:

| Question Number | Answer |
|-----------------|--------|
| (i)             |        |
| (ii)            |        |
| (iii)           |        |
| (iv)            |        |
| (v)             |        |

(For the rough work of these questions use the last page of your answer-sheet or last page of supplement attached)

(i) The forward current through a silicon-based PN junction diode is measured to be 5 mA for a particular Q-point at 300 K. Consider the emission coefficient equal to 2, and compute the dynamic resistance of the diode in  $\Omega$ . [3 M]

(ii) For a NPN BJT,  $\alpha = 0.98$  and collector-base junction reverse bias saturation current ( $I_{CO}$ ) = 0.6  $\mu$ A. This BJT is connected in the common emitter mode and operated in the active region with a base drive current ( $I_B$ ) = 30  $\mu$ A. Find the accurate value of collector current (considering the reverse bias saturation current) for this mode of operation in  $\mu$ A. [3 M]

(iii) The drain current of an n-channel enhancement mode MOSFET drain is shorted to the gate so that  $V_{GS} = V_{DS}$ . The threshold voltage of the MOSFET is 1V. If the drain current is 1mA for  $V_{GS} = 2$ V then for  $V_{GS} = 5$  V find the value of drain current  $I_D$  in mA. [3 M]

(iv) An ideal single-phase ac source of 50 Hz, 230 V (rms) supplies 20 A (rms) to a load at power factor of 0.7 lagging. Write the load impedance in **polar form**. [3 M]

(v) The B-H curve of a magnetic core has value of flux-intensity of 600 AT/m corresponding to flux-intensity of 0.7 T. Calculate value of **relative permeability** of core. [3 M]

-----\*\*\*\*\*-----